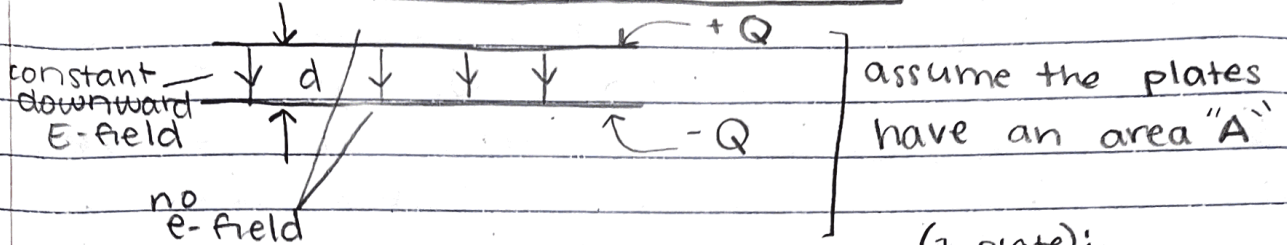


Capacitance: $C = \frac{Q}{V}$ w/units $1F = 1 \frac{C}{V} = \frac{1C^2 s^2}{kg m^2}$ 2/20/23
 quite large
 (typically look at microfarads)

GEOMETRY MATTERS: ▽


ex: (ideal) parallel plate capacitor:





magnitude of e-field btwn plates:

(1 plate): $\oint \vec{E} \cdot d\vec{a} = \frac{Q_{enc}}{\epsilon_0} \rightarrow 2EA$
 $E = \frac{\sigma}{2\epsilon_0}$

(1 plate):

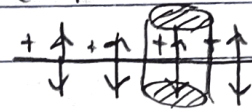

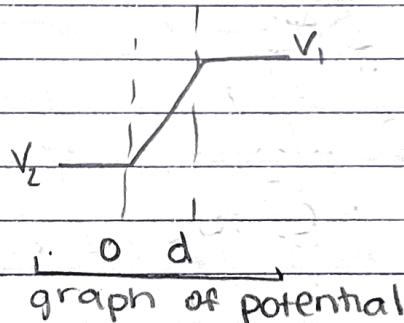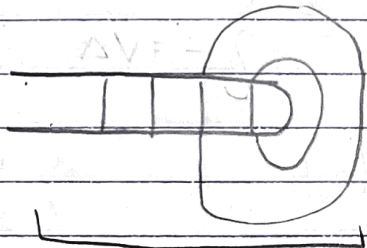Therefore for 2-plates: $E = \frac{2\sigma}{2\epsilon_0} = \frac{\sigma}{\epsilon_0}$



$$\Delta V = - \int \vec{E} \cdot d\vec{a}$$

$$= -E(-d)$$

$$= \frac{\sigma d}{\epsilon_0}$$

e-field lines of capacitor

graph of potential

$C = \frac{Q}{\Delta V} = \frac{\epsilon_0 Q}{\sigma d} = \frac{\epsilon_0 Q A}{Q d} = \frac{\epsilon_0 A}{d}$ solution for capacitance of a parallel plane capacitor

- * C always has E
- * It depends on geometry/shape
- * has length scale (ex: $\frac{A}{d}$)

example 2: spherical shell cap:

$E = \frac{1}{4\pi\epsilon_0} \frac{Q}{r^2}$


$\Delta V = - \int \vec{E} \cdot d\vec{l} = - \int_b^a \left(\frac{1}{4\pi\epsilon_0} \right) \left(\frac{Q}{r^2} \right) dr$

$= - \left(\frac{Q}{4\pi\epsilon_0} \right) \left[\frac{1}{r} \right]_a^b = \left(\frac{Q}{4\pi\epsilon_0} \right) \left(\frac{1}{a} + \frac{1}{b} \right)$

$= \left(\frac{Q}{4\pi\epsilon_0} \right) \left(\frac{b-a}{ab} \right)$


Capacitance from book

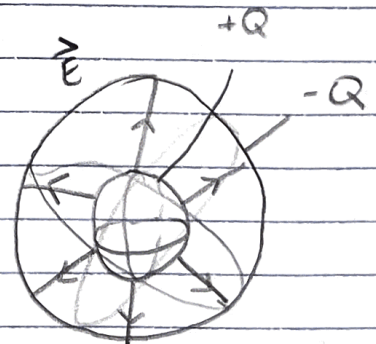$C = \frac{Q}{\Delta V} = \left(\frac{4\pi\epsilon_0 Q}{Q} \right) \left(\frac{ab}{b-a} \right) = \frac{4\pi\epsilon_0 ab}{a-b}$



* DNE can compute "C" for arbitrary configurations of conductors *

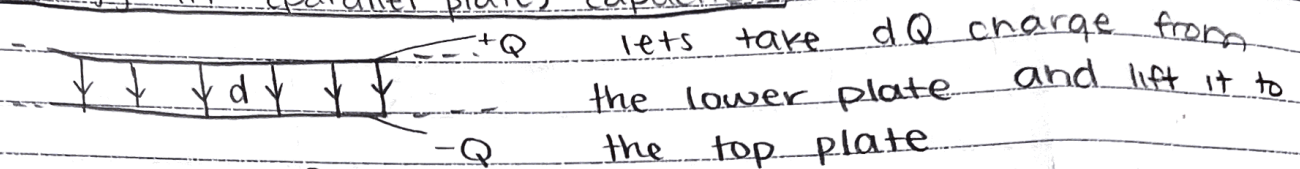→ C is found in a pairwise, C_{12} , fashion energy in (parallel plate) capacitors:



the work $dW = VdQ = \frac{Q}{C} dQ$

for total charge Q : $W = \int_0^Q dW = \int_0^Q \frac{1}{C} Q dQ = \left(\frac{1}{C}\right) \int_0^Q Q dQ = \boxed{\left(\frac{1}{C}\right) \left(\frac{Q^2}{2}\right) = U}$ Potential energy

different forms:

$$U = \left(\frac{1}{C}\right) \left(\frac{Q^2}{2}\right) = \frac{1}{C} \left(\frac{C^2 V^2}{2}\right) = \boxed{\frac{1}{2} C V^2}$$

for parallel plate capacitors:

$$U = \left(\frac{1}{2}\right) \left(\frac{\epsilon_0 A}{d}\right) (Ed)^2 = \left(\frac{1}{2}\right) (\epsilon_0) (Ad) (E^2)$$

⇒ the energy density of the electric volume field is $\boxed{\frac{1}{2} \epsilon_0 E^2}$

$$\vec{F} = -\nabla U \rightarrow \text{for 1D: } F_x = \frac{dU}{dx}$$

apply a force to change the capacitor

$$F_{\text{applied}} = \frac{d}{dx} U = \frac{Q^2 d}{2 dx} \left(\frac{1}{\epsilon}\right)$$

⇒ to change the shape of C

★ MID-TERM:
 Thursday evening
 7pm
 → review soon!

2/22/23

last time: capacitors:

* what is the capacitance?

→ for parallel plate capacitors ||:


$$C = \frac{\epsilon_0 A}{d} \rightarrow \frac{\epsilon A}{d} = \frac{\epsilon_0 (1 + \chi) A}{d}$$

with dielectric material

→ in circuits: $Q = CV$

→ energy stored in capacitors: $U = \frac{1}{2} \frac{Q^2}{C}$

Today: Tour of circuits

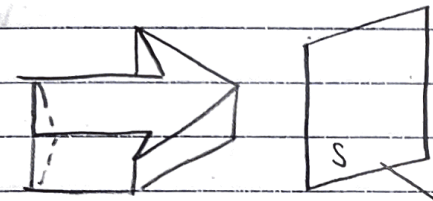

$$I = \int_S \vec{J} \cdot d\vec{a}$$

current

$$\vec{\nabla} \cdot \vec{J} + \frac{\partial \rho}{\partial t} = 0$$

continuity equation
 charge density

\vec{J} = current density surface

- generally: $\vec{J} = \sigma \vec{E}$ (locally)

! NOT CHARGE = CONDUCTIVITY !

$$I = \frac{V}{R}$$

(across an entire wire; globally)

units:

$$V = IR$$

$$R = \text{Ohm} = \Omega = \frac{1V}{1\text{amp}} = \frac{1 \text{kgm}^2}{\text{Cs}}$$




OHM'S LAWS

- any bit of conductor that is not a superconductor has some sort of resistance.

→ charge going through a resistor:

for a little charge flow in dt:

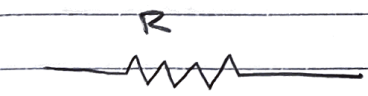


$$U = (Idt)v = (Idt)IR$$

$$dQ = Idt$$

$$\text{power} = P = \frac{dU}{dt} = I^2 R$$


Battery drawn like this!

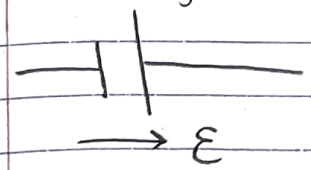

(will come back to batteries in more depth later in semester!)

combining circuit elements:

In series:

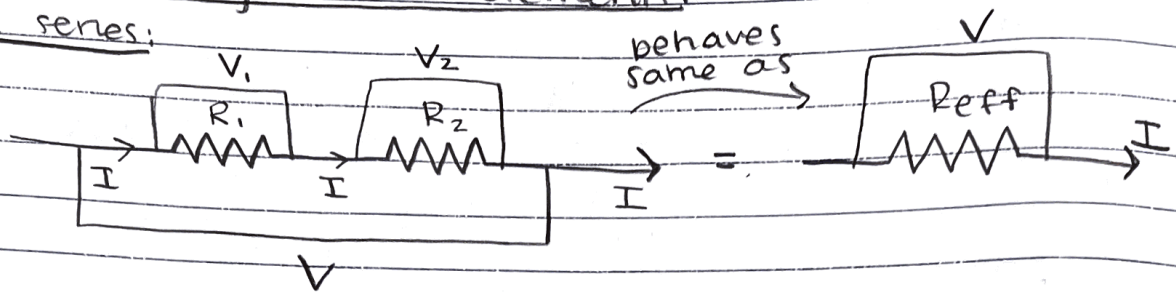

$$V = IR_{\text{eff}} = IR_1 + IR_2$$

$$V = V_1 + V_2$$


★ In series, resistance is added directly ★

currents are constant;

$$R_{\text{eff}} = R_1 + R_2$$

(for resistors in series)

In parallel:

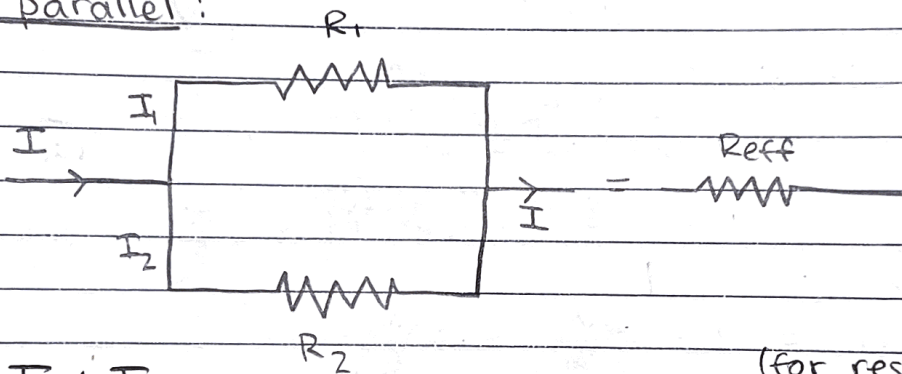

$$I = I_1 + I_2$$

$$V = V_1 = V_2$$

$$V = IR$$

$$\Rightarrow \frac{V}{R_{\text{eff}}} = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow$$

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

(for resistors in parallel)

★ In parallel, resistance is added inversely ★

KIRCHHOFF'S RULES

1) resistors behave as $V = IR$


2) for every node, currents are conserved

3) for every loop, voltages sum to zero ($\oint \vec{E} \cdot d\vec{s} = 0$)

Circuit example problems

resistor + capacitor (one loop)

①

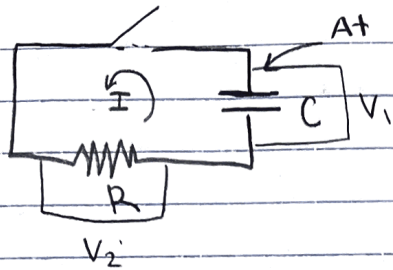

At $t=0$, charged at Q_0


$$V_1 = \frac{Q}{C}$$

$$\frac{Q}{C} + IR = 0$$

$$V_2 = IR$$

but, $I = \frac{dQ}{dt}$, which implies:

graphically:

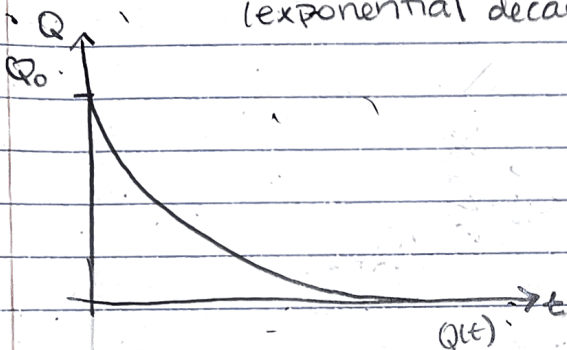

(exponential decay)

$$\frac{dQ}{dt} + \frac{Q}{RC} = 0$$

$$\frac{dQ}{dt} = -\frac{Q}{RC} \Rightarrow \frac{dQ}{Q} = -\frac{dt}{RC}$$

$$= \int_{Q_0}^{Q(t)} \frac{dQ}{Q} = -\int_{0}^{t} \frac{dt}{RC}$$

$$= \ln(Q) \Big|_{Q_0}^{Q(t)} = -\frac{t}{RC}$$


$$\ln(Q) \Big|_{Q_0} = \ln(Q(t)) - \ln(Q_0)$$

$$= \ln\left(\frac{Q(t)}{Q_0}\right)$$

$$\Rightarrow \text{exponentiate: } \frac{Q(t)}{Q_0} = e^{-\frac{t}{RC}}$$

$$Q(t) = Q_0 e^{-\frac{t}{RC}}$$

② resistors + capacitors (two loops)

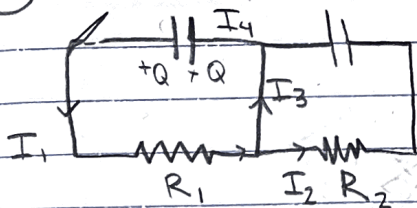

$$I_1 = I_2 + I_3$$

$$I_1 = I_4$$

loops

$$\frac{Q}{C} + IR = 0$$

$$\frac{Q_2}{C} + IR_2 = 0$$

$$I_3 = I_1 - I_2$$

$$I = \frac{dQ}{dt}$$

$$V_1 + V_2 = 0$$

$$V_3 + V_4 = 0$$


$$\frac{Q_1}{C} + IR_1 = \frac{Q_2}{C} + IR_2 = 0$$

* signs for R: potential drops across resistors

- IR if in direction of I

+ IR if in opposite direction of I

example continued w/a resistor:

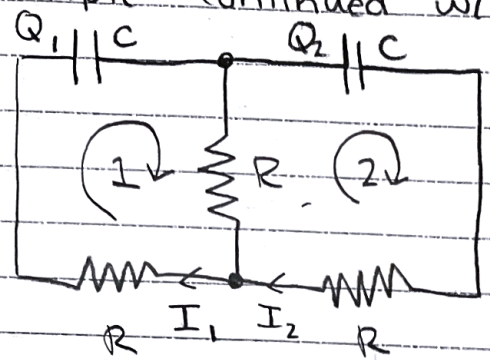

nodes: $I_1 = I_2 + I_3 \Rightarrow I_3 = I_1 - I_2$

loops:
$$\begin{cases} -I_1 R + \frac{Q_1}{C} - I_3 R = 0 \\ -I_2 R + I_3 R + \frac{Q_2}{C} = 0 \end{cases}$$

$I = I_1 + I_2$
 $Q = Q_1 + Q_2$

adding +
$$\begin{cases} -I_1 R + \frac{Q_1}{C} - (I_1 - I_2) R = 0 \\ -I_2 R + (I_1 - I_2) R + \frac{Q_2}{C} = 0 \end{cases}$$

expect a solution like $Q = Q_{sum} e^{-\frac{t}{RC}}$ at:

$$-(I_1 + I_2) R + \frac{Q_1 + Q_2}{C} = 0$$

 last:
$$IR + \frac{Q}{C} = 0$$

subtracting:

$$= (-I_1 + I_2) R + \frac{Q_1 - Q_2}{C} - 2(I_1 - I_2) R = 0$$

$$= 3(I_1 - I_2) R + \frac{Q_1 - Q_2}{C} = 0$$

This means:
 $Q_1(t) = a e^{-\frac{t}{RC}} + b e^{-\frac{t}{3RC}}$
 $Q_2(t) = a e^{-\frac{t}{RC}} - b e^{-\frac{t}{3RC}}$

$$3IR + \frac{Q}{C} = 0$$

$$Q_s = Q_{diff} e^{-\frac{t}{3RC}}$$


 similar expected solution as for adding

at $t=0$
 $Q_1(0) = Q_0 = a + b$
 $Q_2(0) = 0 = a - b$

Therefore:
 final solutions ∇

$$Q_1(t) = \left(\frac{Q_0}{2}\right) \left(e^{-\frac{t}{RC}} + e^{-\frac{t}{3RC}} \right)$$
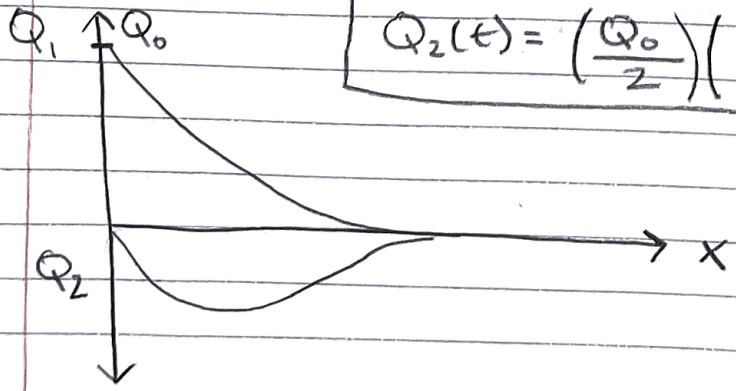
$$Q_2(t) = \left(\frac{Q_0}{2}\right) \left(e^{-\frac{t}{RC}} - e^{-\frac{t}{3RC}} \right)$$



graphically looks like this

special relativity:

based on:

→ the speed of light is independent on the motion of source and observer

= consistency of c

→ "Nature phenomena run their course according to exactly the same general laws... in all inertial reference frame"



= relativity principle

results:

- time dialation
- length contraction
- loss of simultaneity

What is simultaneous?

space-time diagrams:

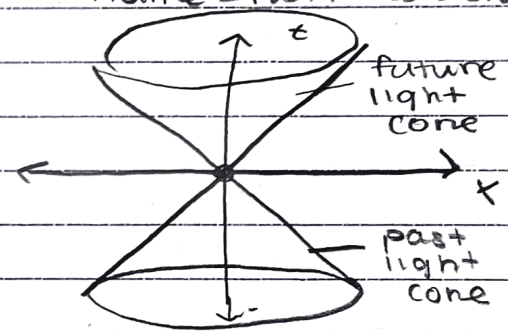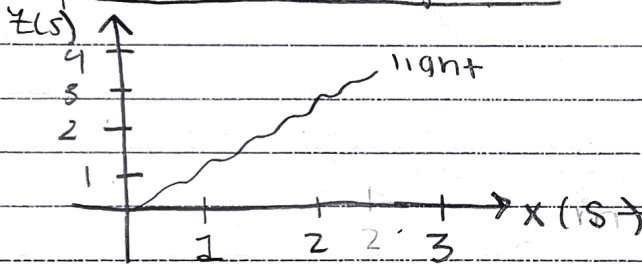


* inertial reference frame = non-acceleration

light-seconds! yay!

* light travels on diagonal lines in s-t diagrams

example: I part I

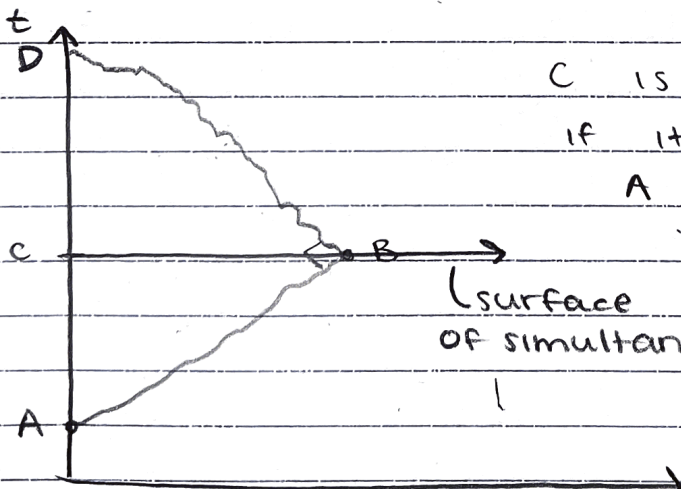

C is simultaneous with B if it is halfway between A and D:


$$T_c = \frac{T'' - T}{2} + 2$$

(surface of simultaneity)


$$= \frac{T'' + T}{2} = T_B$$

rely on c being constant

cont. example: t' 1 part 2

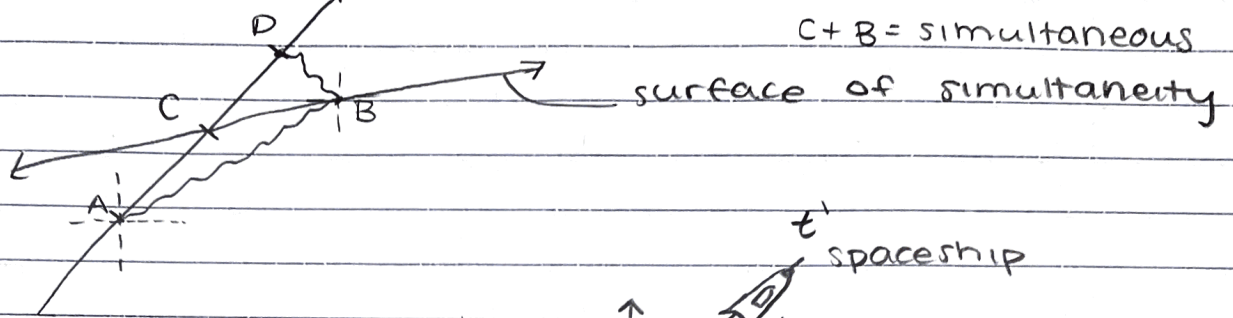

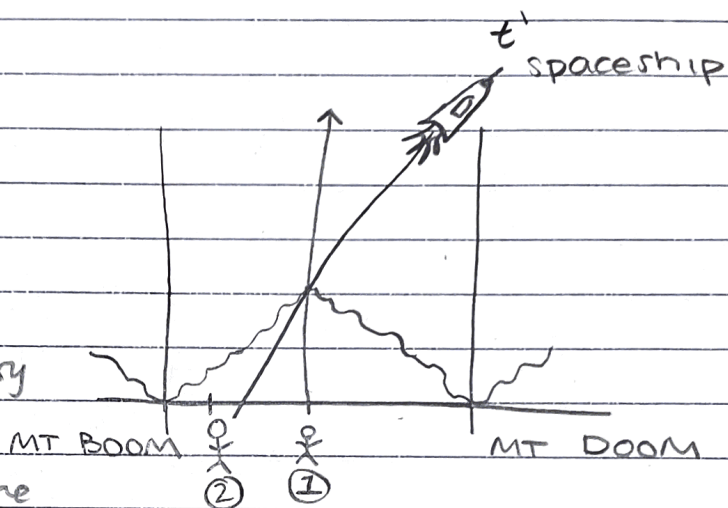puzzle:
two volcanoes
erupt at same
time on either
side of stationary
observer



⇒ eruptions are
simultaneous ①

⇒ BOOM = first then DOOM, seeing light, still times
= simultaneous ②